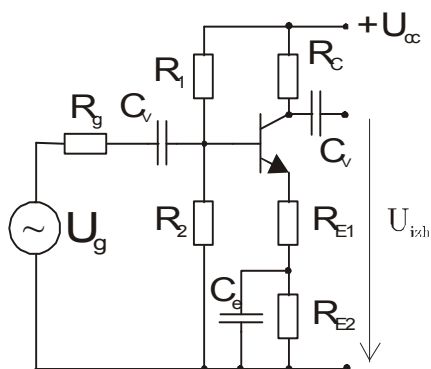


Komunikacijska vezja - rešitve nalog 9.2.2012

1. Izračunajte spodnjo mejno frekvenco in popačenje!



$$\text{Par}(R1, R2) := \frac{R1 \cdot R2}{R1 + R2} \quad U_g := 0.1$$

$$R1 := 40000 \quad R_c := 5000$$

$$R2 := 4000 \quad R_{e1} := 200$$

$$C_e := 50 \cdot 10^{-6} \quad R_{e2} := 1000$$

$$C_v := 5 \cdot 10^{-6} \quad R_g := 3000$$

$$\beta := 100 \quad U_{cc} := 20 \quad U_{be0} := 0.6$$

$$R_B := \text{Par}(R1, R2) \quad R_B = 3.636 \cdot 10^3$$

$$I_e := \frac{U_{cc} \cdot \frac{R2}{R1 + R2} - U_{be0}}{R_{e1} + R_{e2} + \frac{R_B}{\beta + 1}} \quad I_e = 9.856 \cdot 10^{-4} \quad g_m := 40 \cdot I_e \quad r_{be} := \frac{\beta}{g_m}$$

$$R_{vh} := \text{Par}(R_B, r_{be} + R_{e1} \cdot \beta) \quad g_m = 0.039 \quad r_{be} = 2.537 \cdot 10^3$$

$$R_{vh} = 3.131 \cdot 10^3$$

$$A_0 := \left(g_m \cdot R_c \cdot \frac{r_{be}}{r_{be} + \beta \cdot R_{e1}} \right) \cdot \frac{R_{vh}}{R_{vh} + R_g} \quad A_0 = 11.33 \quad 20 \cdot \log(A_0) = 21.085$$

$$R_{nv} := (\text{Par}(R_B, r_{be} + (R_{e1} + R_{e2}) \cdot \beta + r_{be})) + R_g \quad R_{nv} = 6.534 \cdot 10^3$$

$$R_{ne} := \text{Par}(R_{e2} \cdot \beta, R_{e1} \cdot \beta + r_{be} + \text{Par}(R_B, R_g)) \quad R_{ne} = 1.947 \cdot 10^4$$


$$f_{pv} := \frac{1}{2 \cdot \pi \cdot R_{nv} \cdot C_v} \quad f_{pv} = 4.872$$

$$f_{pe} := \frac{\beta + 1}{2 \cdot \pi \cdot C_e \cdot R_{ne}} \quad f_{pe} = 16.511 \quad f_{ne} := \frac{1}{2 \cdot \pi \cdot R_{e2} \cdot C_e} \quad f_{ne} = 3.183$$

$$U_{be} := U_g \cdot \left[\left(\frac{r_{be}}{r_{be} + \beta \cdot R_{e1}} \right) \cdot \frac{R_{vh}}{R_{vh} + R_g} \right] \quad U_{be} \cdot (1000) = 5.748 \quad \text{popačenje je } 5.7\%$$

$$f_{sp} = f_{pe} \quad f_{sp} = 16.511$$

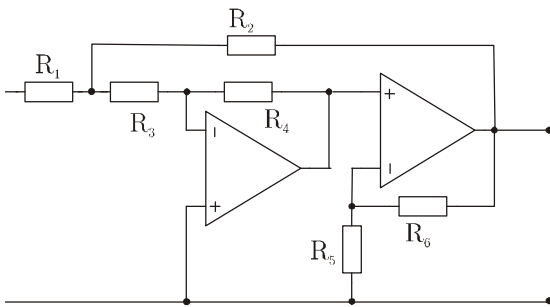2. Izračunajte napetostno ojačenje vezave na sliki !



$R1 := 1000$ $R2 := 25000$
 $R3 := 1000$ $R4 := 25000$
 $R5 := 1000$ $R6 := 25000$
 $A1 := 100$ $A2 := A1$

$$T1 := A1 \cdot \frac{R3}{R3 + R4} \quad Aoz1 := \frac{R4}{R3 + R4} \cdot A1 \quad T2 := A2 \cdot \frac{R5}{R5 + R6} \quad Aoz2 := A2$$

$$T1 = 3.846 \quad Aoz1 = 96.154 \quad T2 = 3.846 \quad Aoz2 = 100$$

$$A\beta1 := \frac{Aoz1}{1 + T1} \quad A\beta1 = 19.841 \quad A\beta2 := \frac{Aoz2}{1 + T2} \quad A\beta2 = 20.635$$


$$Rv1 := R3 + \frac{R4}{1 + A1} \quad Rv1 = 1.248 \cdot 10^3$$

$$T := \frac{\text{Par}(R1, Rv1)}{\text{Par}(R1, Rv1) + R2} \cdot A\beta1 \cdot A\beta2 \quad T = 8.893$$

$$Aoz := \frac{\text{Par}(R2, Rv1)}{R1 + \text{Par}(R2, Rv1)} \cdot (A\beta1 \cdot A\beta2) \quad Aoz = 222.321 \quad A\beta := \frac{Aoz}{1 + T} \quad A\beta = 22.473$$

$$Rvh := R1 + \frac{R2}{1 + A\beta1 \cdot A\beta2} \quad Rvh = 1.061 \cdot 10^3$$

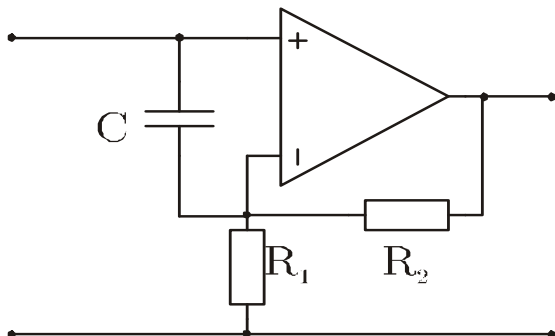2. Izračunajte kompenzacijski kondenzator tako, da bo fazna varnost 60stopinj!
Izračunajte tudi zgornjo mejno frekvenco ojačevalnika !



$$R1 := 1000 \quad R2 := 5000$$

podatki o ojačevalniku:

$$A0 := 10^{\frac{90}{20}} \quad C := 470 \cdot 10^{-9}$$

$$fp1 := 2 \cdot 10^6 \quad fp2 := 30 \cdot 10^6$$

$$T0 := A0 \cdot \frac{R1}{R1 + R2} \quad T0 = 5.27 \cdot 10^3$$

$$fzg := \frac{fp1}{\sqrt{3}} \quad fzg = 1.155 \cdot 10^6 \quad fpk := \frac{fzg}{T0} \quad fpk = 219.089$$

$$C := \frac{1}{2 \cdot \pi \cdot fpk \cdot \text{Par}(R1, R2)} \quad C = 8.717 \cdot 10^{-7}$$