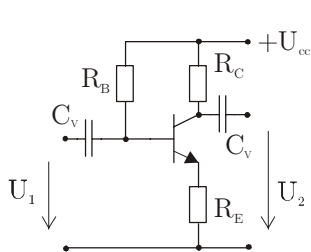


Komunikacijska vezja - rešitve nalog 15.9.2003

1. Izračunajte ojačenje in koeficient nelinearnega popačenja zaradi druge harmonske komponente !



$$\text{Par}(R1, R2) := \frac{R1 \cdot R2}{R1 + R2}$$

$$R_B := 330000 \quad R_C := 5000 \quad R_E := 1000 \quad U_1 := 0.1$$

$$C_V := 10^{-6} \quad U_{CC} := 10 \quad \beta := 100 \quad U_{BE0} := 0.6$$

$$I_e := \frac{U_{CC} - U_{BE0}}{\frac{R_B}{\beta} + R_E}$$

$$I_e = 2.186 \cdot 10^{-3} \quad g_m := 40 \cdot I_e \quad r_{be} := \frac{\beta}{g_m}$$

$$g_m = 0.087 \quad r_{be} = 1.144 \cdot 10^3$$

$$A_u := -g_m \cdot R_C \cdot \frac{r_{be}}{r_{be} + R_E \cdot (\beta + 1)}$$

$$A_u = -4.895$$

$$U_{BE} := U_1 \cdot \frac{r_{be}}{r_{be} + R_E \cdot (\beta + 1)}$$


$$k_2 := U_{BE} \cdot 1000$$

$$k_2 = 1.12$$

2. Izračunajte natančno ojačenje ojačevalnika !

$$R_1 := 1 \quad R_2 := 1 \quad R_3 := 10 \quad R_4 := 100 \quad R_5 := 10 \quad R_6 := 1 \quad R_7 := 1 \quad R_8 := 50$$

$$A := 100$$

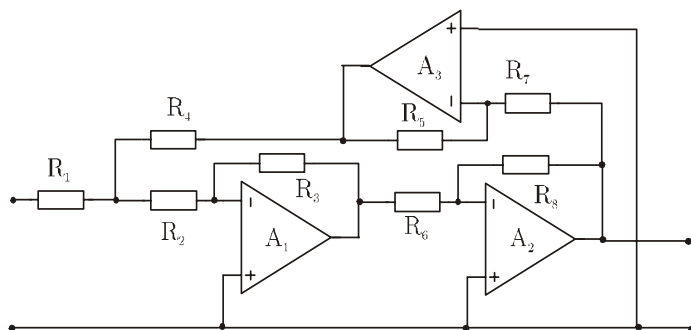

$$T_1 := A \cdot \frac{R_2}{R_2 + R_3} \quad T_1 = 9.091 \quad A_{b1} := \frac{-R_3}{R_2} \quad A_{b1} = -9.009$$

$$1 + \frac{1}{T_1}$$

$$R_{vh1} := R_2 + \frac{R_3}{1 + A} \quad R_{vh1} = 1.099$$

$$T2 := A \cdot \frac{R6}{R6 + R8} \quad T2 = 1.961 \quad Ab2 := \frac{-R8}{1 + \frac{1}{T2}} \quad Ab2 = -33.113$$


$$T3 := A \cdot \frac{R7}{R7 + R5} \quad T3 = 9.091 \quad Ab3 := \frac{-R5}{1 + \frac{1}{T3}} \quad Ab3 = -9.009$$

$$Aoz := \frac{\text{Par}(R4, Rvh1)}{R1 + \text{Par}(R4, Rvh1)} \cdot Ab1 \cdot Ab2 \quad Aoz = 155.378$$

$$T := - \left[\frac{\text{Par}(R1, Rvh1)}{(R4 + \text{Par}(R1, Rvh1))} \cdot Ab1 \cdot Ab2 \cdot Ab3 \right] \quad T = 13.998$$

$$Ab := \frac{Aoz}{1 + T} \quad Ab = 10.36$$

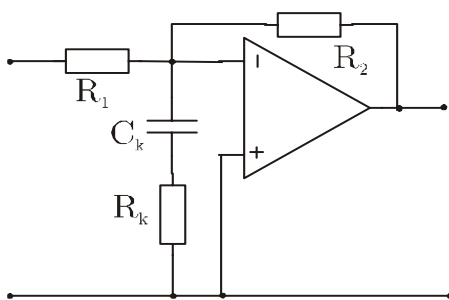3. Ojačevalnik kompenzirajte s polom in ničlo tako, da bo fazna varnost 45 stopinj!



$$\Phi_m := \frac{\pi}{4}$$

$$R1 := 10000 \quad R2 := 100000$$

podatki o ojačevalniku:

$$A0 := 10^5$$

$$fp1 := 5 \cdot 10^5 \quad fp2 := 5 \cdot 10^6$$

$$T0 := A0 \cdot \frac{R1}{R1 + R2} \quad T0 = 9.091 \cdot 10^3 \quad f_{zg} := fp2 \quad f_{pk} := \frac{f_{zg}}{T0} \quad f_{nk} := fp1$$

$$f_{pk} = 550 \quad f_{nk} = 5 \cdot 10^5$$

$$\text{ničla : } \frac{1}{2 \cdot \pi \cdot Ck \cdot Rk} \quad \text{pol : } \frac{1}{2 \cdot \pi \cdot Ck \cdot (Rk + R1)} \quad Rk := \frac{R1}{\frac{f_{nk}}{f_{pk}} - 1} \quad Rk = 11.012$$

$$Ck := \frac{1}{2 \cdot \pi \cdot Rk \cdot f_{nk}} \quad Ck = 2.891 \cdot 10^{-8}$$