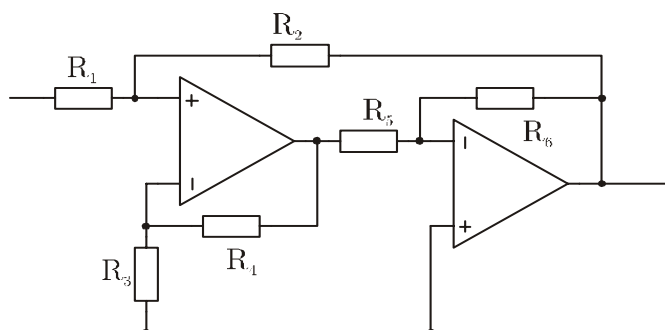


Komunikacijska vezja - rešitve nalog 26.1.2004

1. Izračunajte vhodno upornost in napetostno ojačenje vezave na sliki !



$$\text{Par}(R1, R2) := \frac{R1 \cdot R2}{R1 + R2}$$

$$R1 := 1000 \quad R2 := 10000$$

$$R3 := 1000 \quad R4 := 10000$$

$$R5 := 1000 \quad R6 := 10000$$

$$A1 := 100 \quad A2 := 100$$

$$T1 := A1 \cdot \frac{R3}{R3 + R4} \quad \text{Aoz1} := A1$$

$$T1 = 9.091 \quad \text{Aoz1} = 100$$

$$A\beta1 := \frac{\text{Aoz1}}{1 + T1} \quad A\beta1 = 9.91$$

$$T2 := A2 \cdot \frac{R5}{R5 + R6} \quad \text{Aoz2} := \frac{R6}{R5 + R6} \cdot A2$$

$$T2 = 9.091 \quad \text{Aoz2} = 90.909$$


$$A\beta2 := \frac{\text{Aoz2}}{1 + T2} \quad A\beta2 = 9.009$$

$$T := \frac{R1}{R1 + R2} \cdot A\beta1 \cdot A\beta2 \quad T = 8.116$$

$$\text{Aoz} := \frac{R2}{R1 + R2} \cdot (A\beta1 \cdot A\beta2) \quad \text{Aoz} = 81.162 \quad A\beta := \frac{\text{Aoz}}{1 + T} \quad A\beta = 8.903$$

$$R_{vh} := R1 + \frac{R2}{1 + A\beta1 \cdot A\beta2} \quad R_{vh} = 1.111 \cdot 10^3$$

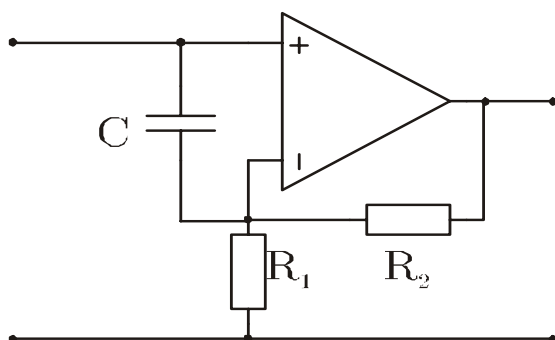2. Ojačevalnik kompenzirajte tako, da bo fazna varnost 60 stopinj! Izračunajte zgornjo mejno frekvenco ojačevalnika !



$$\Phi_m := \pi \cdot \frac{60}{180}$$

$$R1 := 10000 \quad R2 := 90000$$

podatki o ojačevalniku:

$$A0 := 10^6$$


$$f_{p1} := 2 \cdot 10^6 \quad f_{p2} := 20 \cdot 10^6$$

$$T0 := A0 \cdot \frac{R1}{R1 + R2} \quad T0 = 1 \cdot 10^5 \quad f_{zg} := \frac{f_{p1}}{\sqrt{3}} \quad f_{zg} = 1.155 \cdot 10^6$$

$$f_{pk} := \frac{f_{zg}}{T0} \quad f_{pk} = 11.547 \quad \theta := \frac{180}{\pi} \cdot \left(\text{atan}\left(\frac{f_{zg}}{f_{p1}}\right) + \text{atan}\left(\frac{f_{zg}}{f_{p2}}\right) \right) \quad \theta = 123.304$$

$$C := \frac{1}{2 \cdot \pi \cdot f_{pk} \cdot \text{Par}(R1, R2)} \quad C = 1.531 \cdot 10^{-6}$$

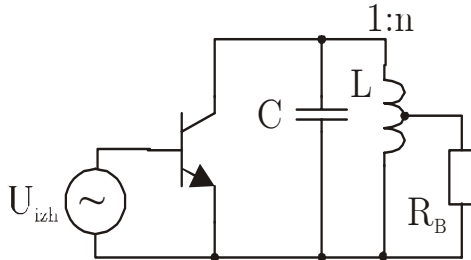2. Izračunajte ojačenje in pasovno širino selektivnega ojačevalnika, če je induktivni sklop breme optimalen !



$$C22 := 3 \cdot 10^{-12}$$

$$Q_{ok} := 150$$

$$g22 := 10 \cdot 10^{-6}$$

$$g21 := 40 \cdot 10^{-3}$$

$$L := 10 \cdot 10^{-6}$$

$$R_B := 5 \cdot 10^3$$

$$C := 100 \cdot 10^{-12}$$

$$\omega_0 := \frac{1}{\sqrt{L \cdot (C + C22)}}$$

$$g_k := \frac{1}{Q_{ok} \cdot \omega_0 \cdot L}$$

$$g_k = 2.14 \cdot 10^{-5}$$

$$n := \sqrt{g22 \cdot R_B}$$

$$n = 0.224$$

$$f_0 := \frac{\omega_0}{2 \cdot \pi} \quad f_0 = 4.959 \cdot 10^6$$

$$Q_{eff} := Q_{ok} \cdot \frac{g_k}{g_k + 2 \cdot g22}$$

$$B := \frac{f_0}{Q_{eff}}$$

$$Q_{eff} = 77.529$$

$$B = 6.396 \cdot 10^4$$

$$A_0 := \frac{g21}{g_k + 2 \cdot g22} \cdot n$$

$$A_0 = 216.067$$